

Introduction to Computer Architecture: How Computers Add

Fair Use Building and Research
<http://fubarlabs.org>



Introductions!

What is your name?

What brings you here?

Logic Basics: And, Or, Not

It's raining AND it's cloudy

It's sunny OR it's cloudy

It's sunny, NOT cloudy

It's sunny, AND it's NOT raining

Boolean Algebra

http://en.wikipedia.org/wiki/Boolean_algebra

... Boolean algebra is the algebra of truth values 0 and 1...

0 and 1

Yes and No

True and False

+ and -

Red and Black (or Blue)

High and Low

Boolean Algebra Conventions

(one of many!)

$A + B$	A or B
$A.B$... or just AB	A and B
A'	Not A
$(A + B)'$	Not (A or B)
$(AB)'$	Not (A and B)
$A'B'$	(Not A) and (Not B)
$(\text{Sunny}).(\text{Raining})'$	Sunny and Not Raining

Another boolean convention

From: http://en.wikipedia.org/wiki/De_Morgan's_laws

The rules can be expressed in formal language with two propositions P and Q as:

$$\neg(P \wedge Q) \iff (\neg P) \vee (\neg Q)$$
$$\neg(P \vee Q) \iff (\neg P) \wedge (\neg Q)$$

where:

- \neg is the negation operator (NOT)
- \wedge is the conjunction operator (AND)
- \vee is the disjunction operator (OR)
- \iff is a metalogical symbol meaning "can be replaced in a logical proof with"

Truth Tables

AND:

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

Truth Tables - $(AB)'$ vs. $(A'B')$

A	B	A and B	Not (A and B)
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A	B	A'	B'	A' and B'
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

Laws and Theorems of Boolean Algebra

from: <http://www.ee.surrey.ac.uk/Projects/Labview/boolalgebra/index.html>

T1 : Commutative Law

(a) $A + B = B + A$

(b) $A B = B A$

T2 : Associate Law

(a) $(A + B) + C = A + (B + C)$

(b) $(A B) C = A (B C)$

T3 : Distributive Law

(a) $A (B + C) = A B + A C$

(b) $A + (B C) = (A + B) (A + C)$

T4 : Identity Law

(a) $A + A = A$

(b) $A A = A$

... More laws, etc.

from: <http://www.ee.surrey.ac.uk/Projects/Labview/boolalgebra/index.html>

T5 :

- (a) $AB + A\bar{B} = A$
- (b) $(A+B)(A+\bar{B}) = A$

T6 : Redundance Law

- (a) $A + AB = A$
- (b) $A(A+B) = A$

T7 :

- (a) $0 + A = A$
- (b) $0A = 0$

T8 :

- (a) $1 + A = 1$
- (b) $1A = A$

T9 :

- (a) $\bar{A} + A = 1$
- (b) $\bar{A}A = 0$

T10 :

- (a) $A + \bar{A}B = A + B$
- (b) $A(\bar{A} + B) = AB$

De Morgan's Law

$$(AB)' = A' + B'$$

$$(A + B)' = A'B'$$

Proofs with Truth Tables




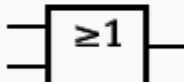

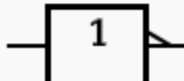
Prove T10(a):

$$A + A'B = A + B$$




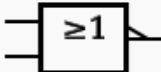

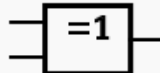

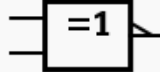
A	B	A'	A + B	A'B	A + A'B
0	0	1	0	0	0
0	1	1	1	1	1
1	0	0	1	0	1
1	1	0	1	0	1

Basic Logic Gates

from: http://en.wikipedia.org/wiki/Logic_gate

Type	Distinctive shape	Rectangular shape	Boolean algebra between A & B	Truth table																		
AND			$A \cdot B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A AND B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	A AND B	0	0	0	0	1	0	1	0	0	1	1	1
INPUT		OUTPUT																				
A	B	A AND B																				
0	0	0																				
0	1	0																				
1	0	0																				
1	1	1																				
OR			$A + B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A OR B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	A OR B	0	0	0	0	1	1	1	0	1	1	1	1
INPUT		OUTPUT																				
A	B	A OR B																				
0	0	0																				
0	1	1																				
1	0	1																				
1	1	1																				
NOT			\overline{A}	<table><tr><th>INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>NOT A</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	INPUT	OUTPUT	A	NOT A	0	1	1	0										
INPUT	OUTPUT																					
A	NOT A																					
0	1																					
1	0																					

NAND, etc.

NAND			$\overline{A \cdot B}$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A NAND B</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	A NAND B	0	0	1	0	1	1	1	0	1	1	1	0
INPUT		OUTPUT																				
A	B	A NAND B																				
0	0	1																				
0	1	1																				
1	0	1																				
1	1	0																				
NOR			$\overline{A + B}$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A NOR B</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	A NOR B	0	0	1	0	1	0	1	0	0	1	1	0
INPUT		OUTPUT																				
A	B	A NOR B																				
0	0	1																				
0	1	0																				
1	0	0																				
1	1	0																				
XOR			$A \oplus B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A XOR B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	A XOR B	0	0	0	0	1	1	1	0	1	1	1	0
INPUT		OUTPUT																				
A	B	A XOR B																				
0	0	0																				
0	1	1																				
1	0	1																				
1	1	0																				
XNOR			$\overline{A \oplus B}$ or $A \odot B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A XNOR B</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	A XNOR B	0	0	1	0	1	0	1	0	0	1	1	1
INPUT		OUTPUT																				
A	B	A XNOR B																				
0	0	1																				
0	1	0																				
1	0	0																				
1	1	1																				

MineCraft Logic Gates



Air
(Null)



Switch
(Input)



Block
(Generic)



Torch
(Side of Block)



Torch
(On Ground)



Torch
(Top of Block)



Redstone
(On Ground)



Redstone
(Top of Block)



Redstone
(Output)



Redstone
(Inverse Output)

Input/Output Gate



NOT Gate
(Inverter)



AND Gate




OR Gate




XOR Gate




Rapid Pulser

 


RS NOR Latch
(Memory Cell)

 

NAND Gate

 


NOR Gate

 


XNOR Gate



RS NAND Latch
(Memory Cell)

 

5-Clock
(Pulser)

 

Repeater



NANDs are "universal gates"

So are NORs -- http://en.wikipedia.org/wiki/NAND_logic

AND from earlier:

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

NAND



Truth Table

Input A	Input B	Output Q
0	0	1
0	1	1
1	0	1
1	1	0

More NAND Gates

Desired Gate



NAND Construction




Truth Table

Input A	Output Q
0	1
1	0

Desired Gate



NAND Construction

 

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1


$$F = (F')'$$

More NAND Gates

OR

[\[edit\]](#)

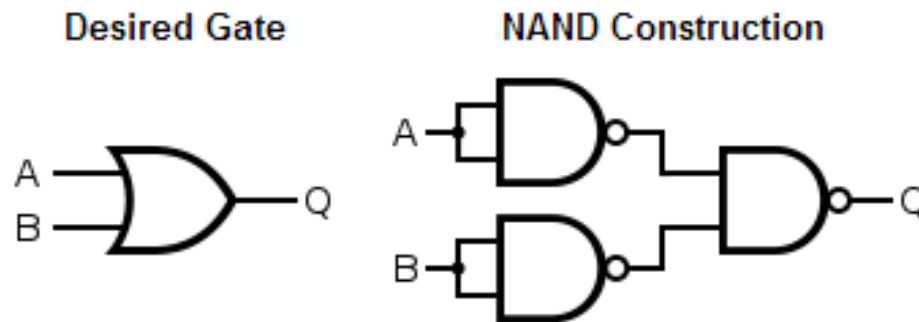If the truth table for a NAND gate is examined or by [applying De Morgan's Laws](#), it can be seen that if any of the inputs are 0, [then the](#) output will be 1. To be an OR gate, however, the output must be 1 if any input is 1. Therefore, if the inputs are inverted, any high input will trigger a high output.



Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1

More NAND Gates

XOR


[\[edit\]](#)

An XOR gate is constructed similarly to an OR gate, except with an additional NAND gate inserted such that if both inputs are high, the inputs to the final NAND gate will also be high, and the output will be low. This effectively represents the formula: "NAND(A NAND (A NAND B)) NAND (B NAND (A NAND B))".

Desired Gate



NAND Construction

 

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	0

XOR - Truth Table to Gates

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	0

WIKI Says:

This effectively represents the formula:
 $\text{NAND}(A \text{ NAND } (A \text{ NAND } B)) \text{ NAND } (B \text{ NAND } (A \text{ NAND } B))$

OR:

$((A.(AB))').(B.(A.B))')$

Karnaugh Maps

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	0

A \ B		0	1
0	0		
	1		

Karnaugh Maps - XOR

A \ B		0	1
	0	0	1
	1	1	0

Sum of Products: SoP

-- Work with the ones, OR them together

Product of Sums: PoS

-- Work with the zeros, AND them together

Karnaugh Maps - XOR

A \ B	0	1
0	0	1
1	1	0

Sum of Products: SoP (1s ORd)

$$F = (A'B) + (AB')$$

Product of Sums: PoS (0s ANDed)

$$F = (A' + B').(A + B)$$

Drawing XOR with Gates

$$F = (A' + B').(A + B)$$

Drawing XOR with NANDs

Simplifying XOR

$$F = (A' + B').(A + B)$$

First: De Morgan's Law!

$$(AB)' = A' + B' \quad \dots F = (AB)'.(A + B)$$

...then T3 : Distributive Law

$$(a) A (B + C) = A B + A C$$

Simplifying XOR

$$F = (AB)' \cdot (A + B)$$

...then T3 : Distributive Law

$$(a) X(Y + Z) = XY + XZ$$

$$F = (AB)'(A) + (AB)'(B)$$

$$F' = ((AB)'(A) + (AB)'(B))'$$

...then remember, $F = (F)'$

... and De Morgan's (other) Law $(A + B)' = A'B'$

Simplifying XOR

$$F = (AB)'(A) + (AB)'(B)$$

...then remember, $F = (F')'$

... and De Morgan's (other) Law $(A + B)' = A'B'$

$$F'' = F = ((AB)'(A) + (AB)'(B))''$$

$$F = ((A(AB)')'.(B.(AB)'))'$$

Simplifying XOR


$$F'' = F = ((AB)'(A) + (AB)'(B))''$$

$$F = ((A(AB)')'.(B.(AB)'))'$$


This effectively represents the formula: "NAND (A NAND (A NAND B)) NAND (B NAND (A NAND B))".

Simplifying XOR - Draw it

NAND Construction



 


Setting up the breadboard

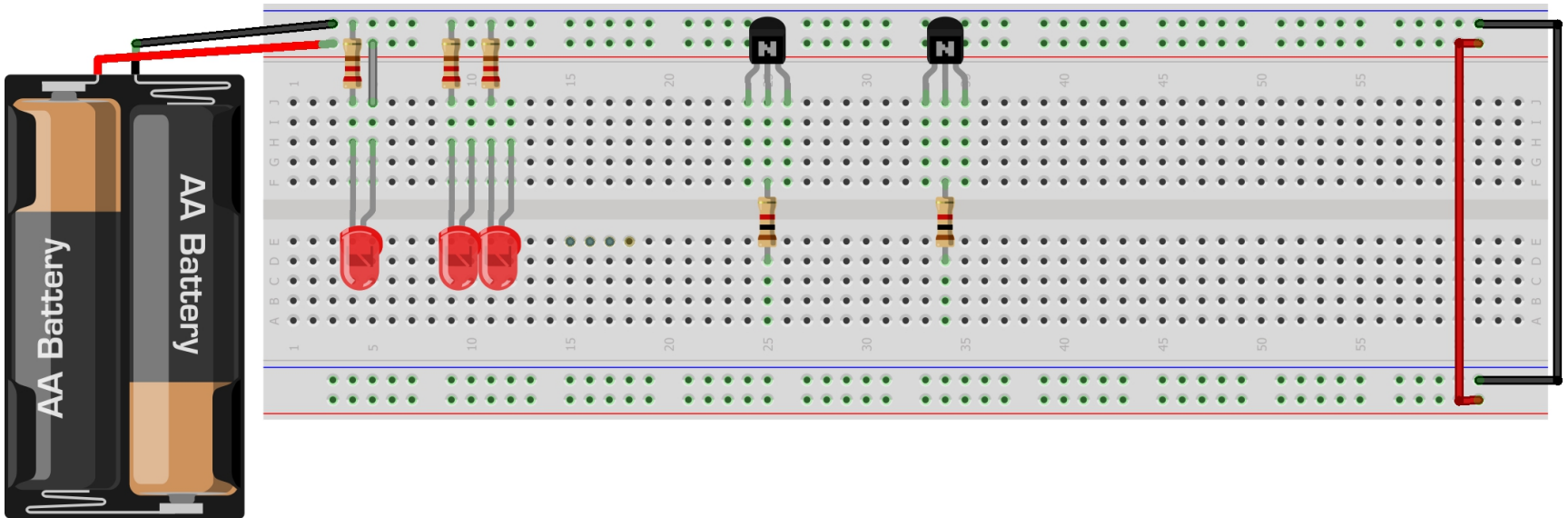


Transistors

   
NPN transistor (Current sink)
(e.g. PN2222)





Transistor Gate - AND

 

TO-92


 


Let's build an AND

 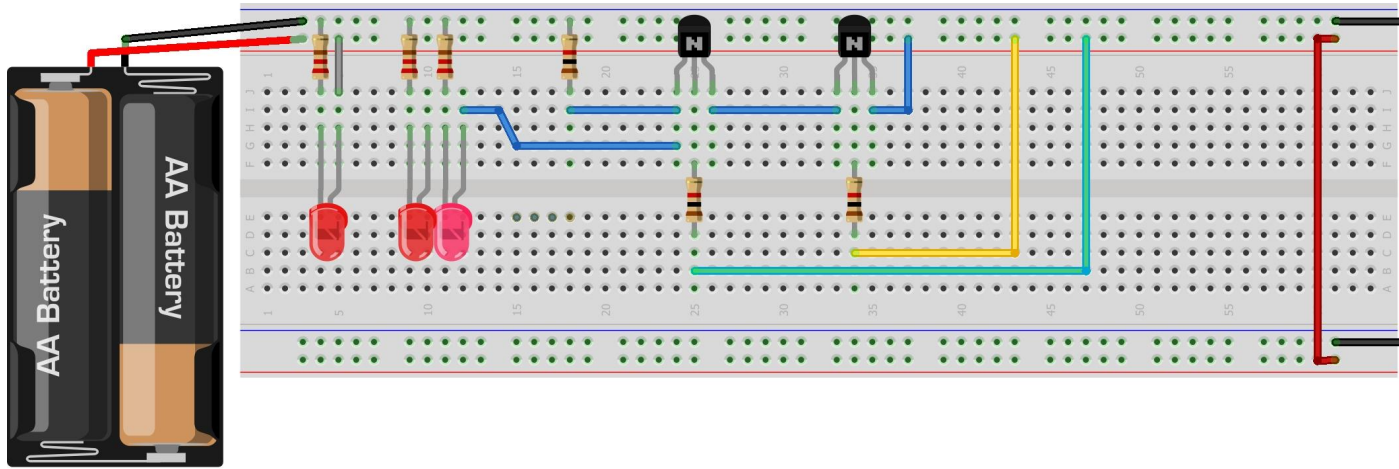

Made with  Fritzing.org


Let's build an OR

 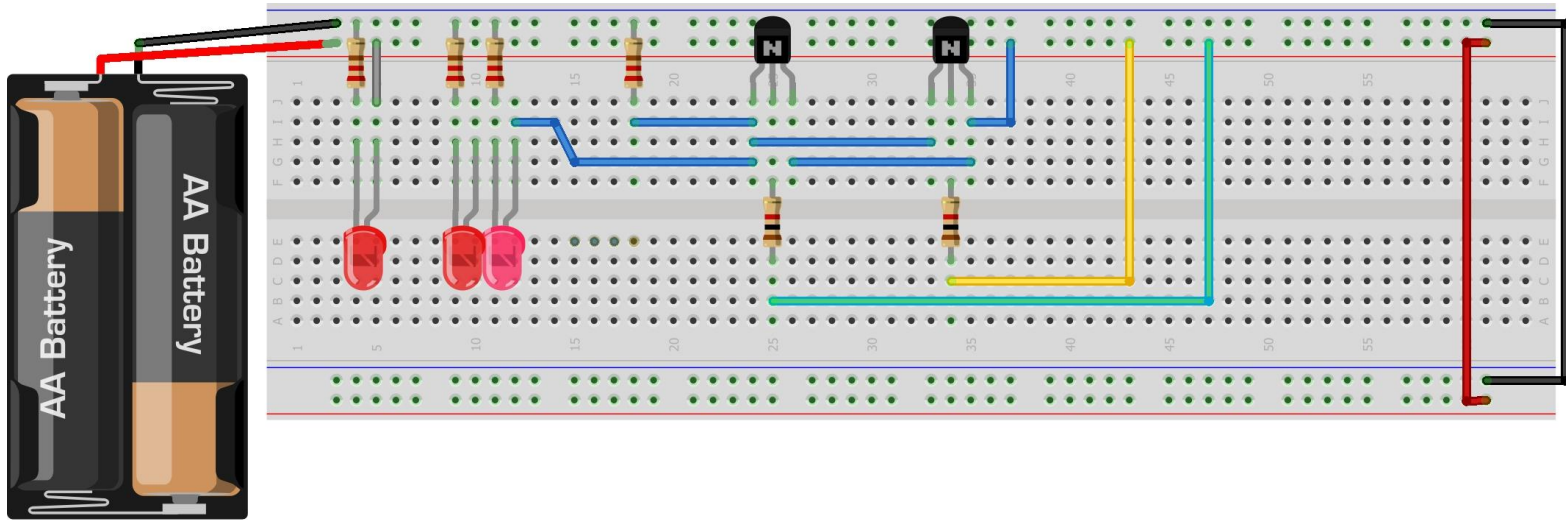



Made with  Fritzing.org

NANDs -- why they are common







AND

 


NAND

  

Presenting: The 7400 Series

     
 


 Note the "backwards" orientation of all four gates on the 74LS02 chip




Note the "backwards" orientation of two of the four gates on the 747266 chip



7400 - Quad, dual input NAND gate

  


Set up the breadboard

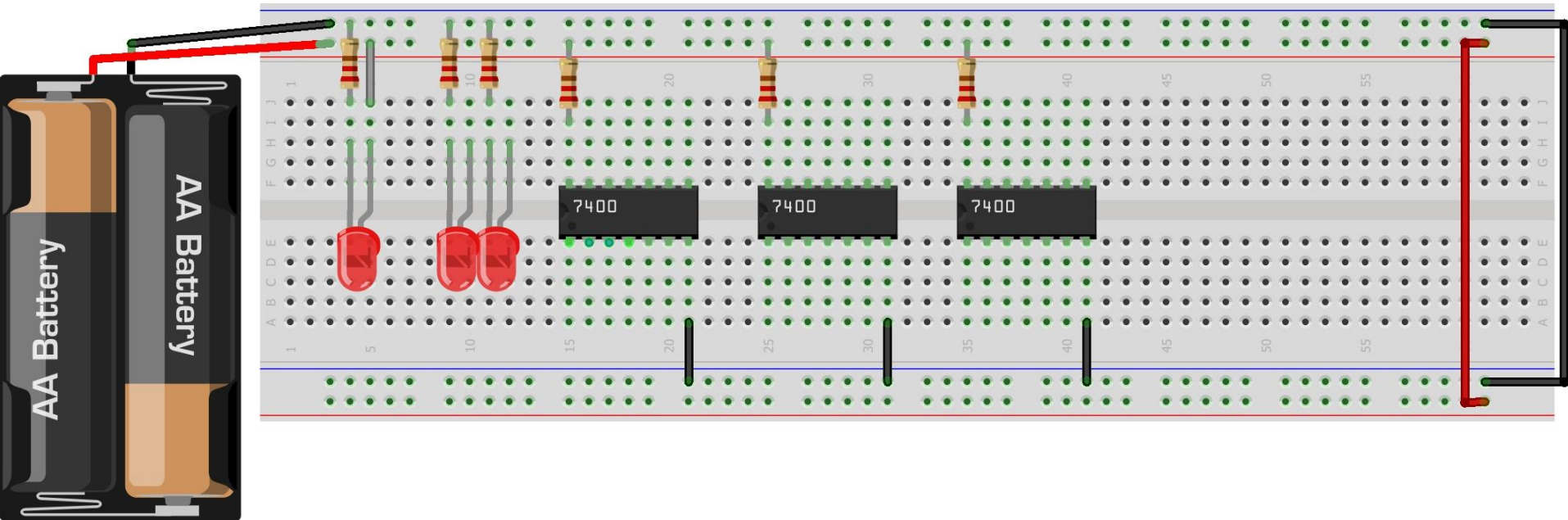


Build a NOT from NAND

 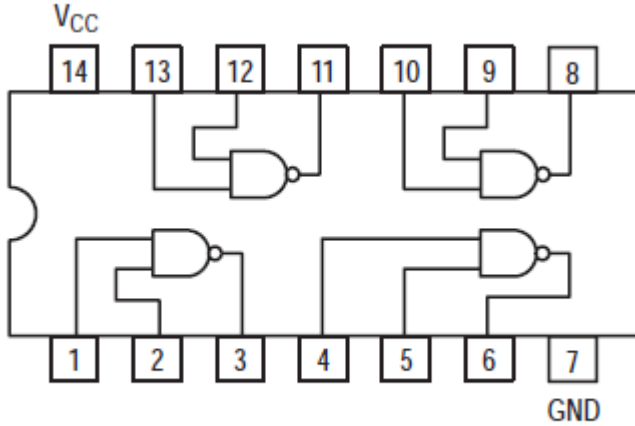

Input A	Output Q
0	1
1	0

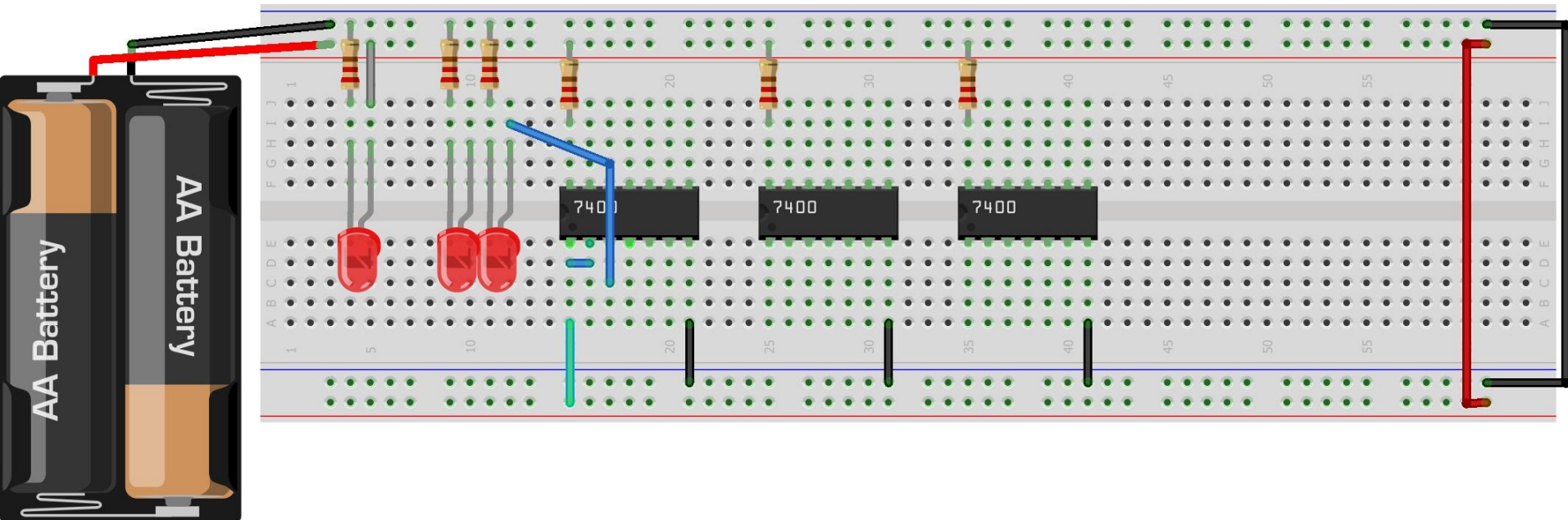


Build an AND from NAND

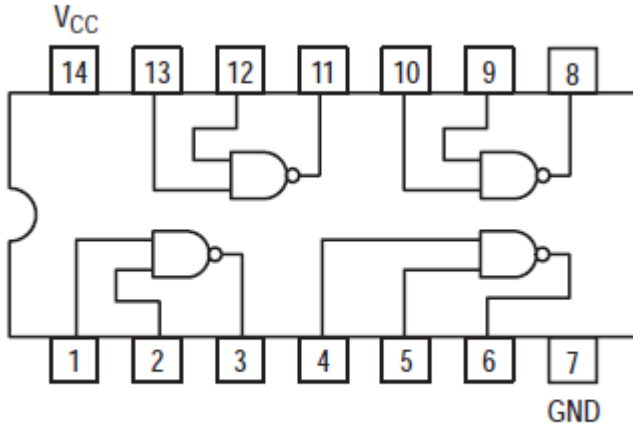

Desired Gate




NAND Construction

 

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1

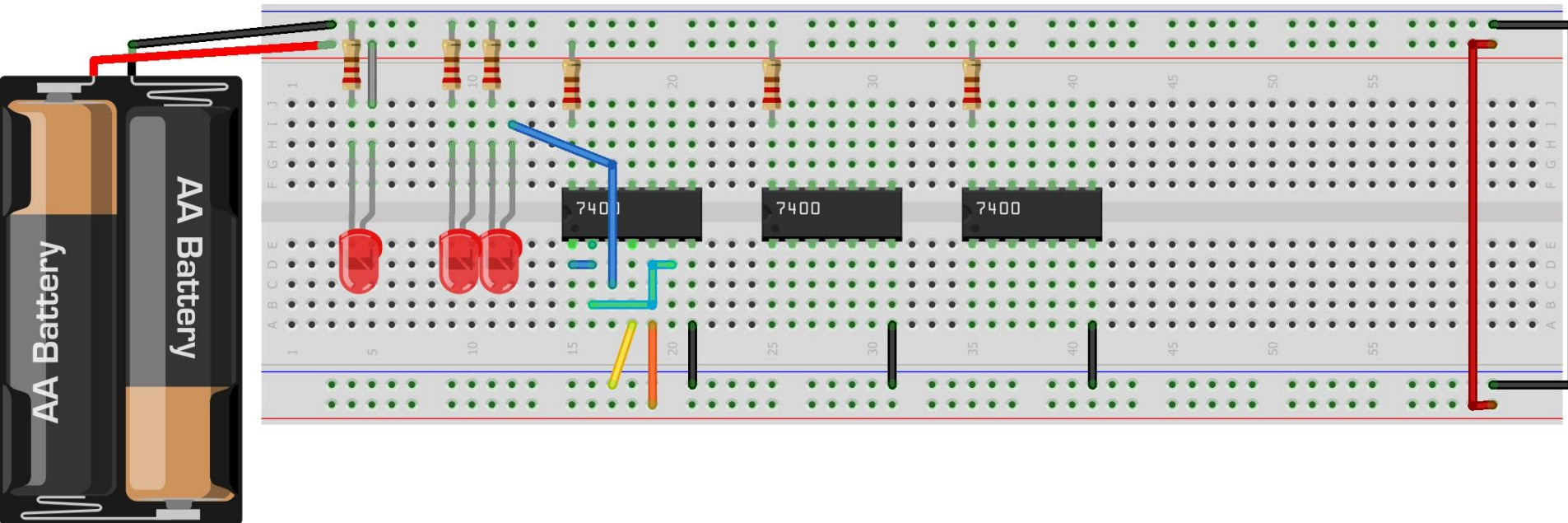

Binary vs. Decimal

from: <http://cs.iupui.edu/~n241/readings/binconv.html>

Number	7	4	0	8
Position Name	Thousands	Hundreds	Tens	Ones
Exponential Expression	10^3*7	10^2*4	10^1*0	10^0*8
Calculated Exponent	$1000*7$	$100*4$	$10*0$	$1*8$

Table 1: Decimal Placeholders

Number	1	1	0	1
Position Name	Eights	Fours	Twos	Ones
Exponential Expression	2^3*1	2^2*1	2^1*0	2^0*1
Calculated Exponent	$8*1$	$4*1$	$2*0$	$1*1$

Table 2: Binary Placeholders

Binary Numbers

0000 = 0	1000 = 8
0001 = 1	1001 = 9
0010 = 2	1010 = 10
0011 = 3	1011 = 11
0100 = 4	1100 = 12
0101 = 5	1101 = 13
0110 = 6	1110 = 14
0111 = 7	1111 = 15

Binary Addition

(+ is back to add, for now!)

$$\begin{array}{r} 0010 \quad (2) \\ + 1011 \quad (11) \\ \hline 1101 \quad (13) \end{array}$$

Binary Addition - just 1 bit

(+ is back to add, for now!)

$$0 + 0 = 0$$

$$0 + 1 = 1$$


$$1 + 0 = 1$$

$$1 + 1 = 0 \quad \dots \quad ?$$



Binary Addition - just 1 bit - Truth Table

A	B	S (Sum, a + b)
0	0	0
0	1	1
1	0	1
1	1	0

Build the XOR!

 

NAND Construction


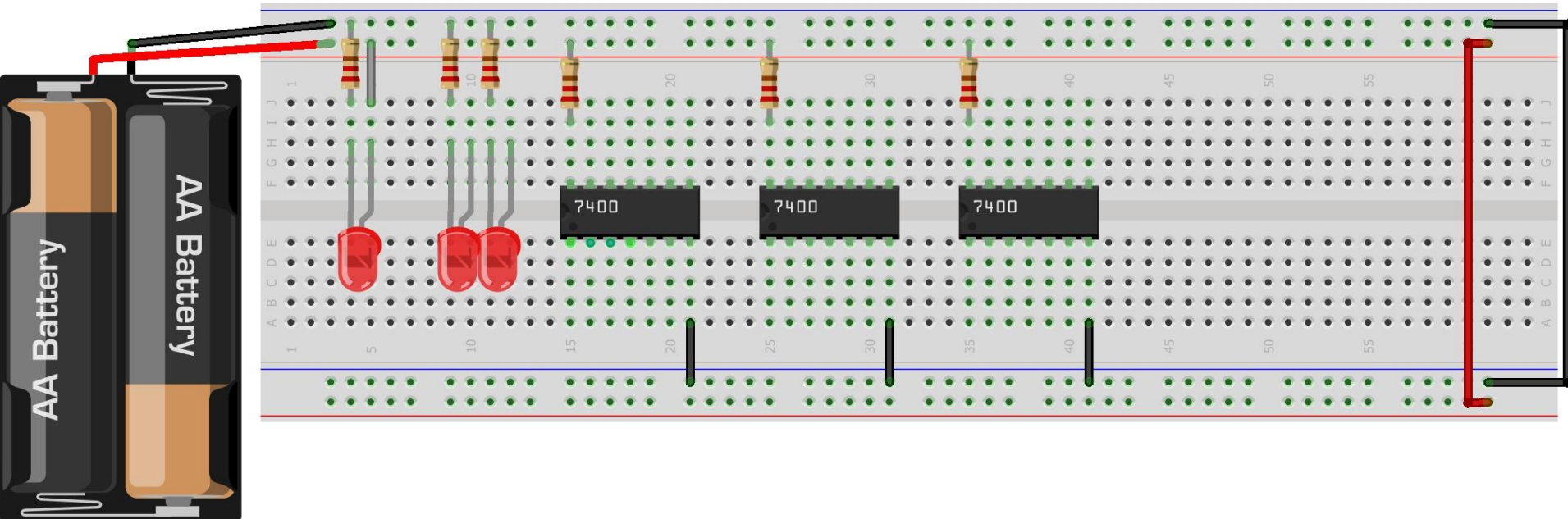
 


Binary Addition - just 1 bit - Truth Table




A	B	C (Carry)
0	0	0
0	1	0
1	0	0
1	1	1

$C = A \cdot B$ (Carry equals A and B)



Build the Half Adder!

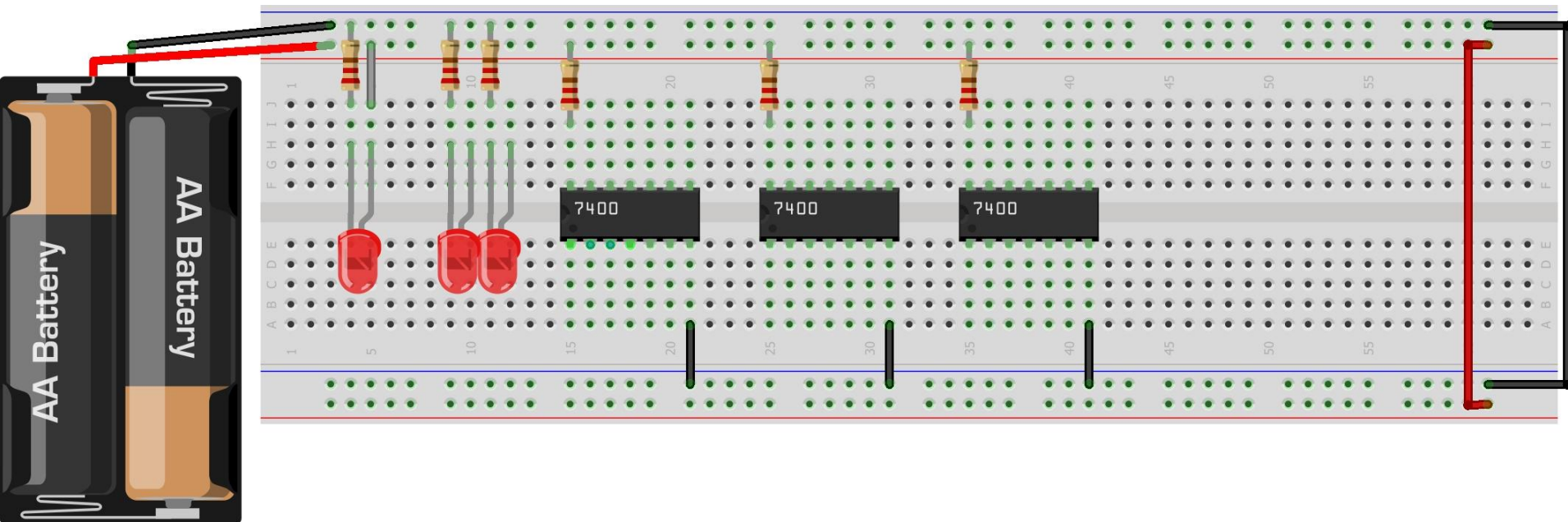 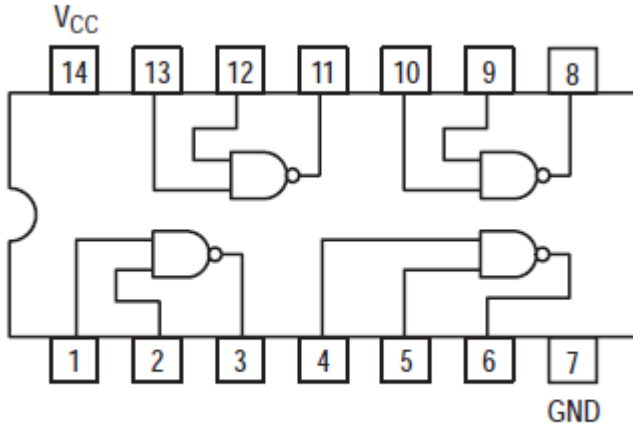

Build the Full Adder!

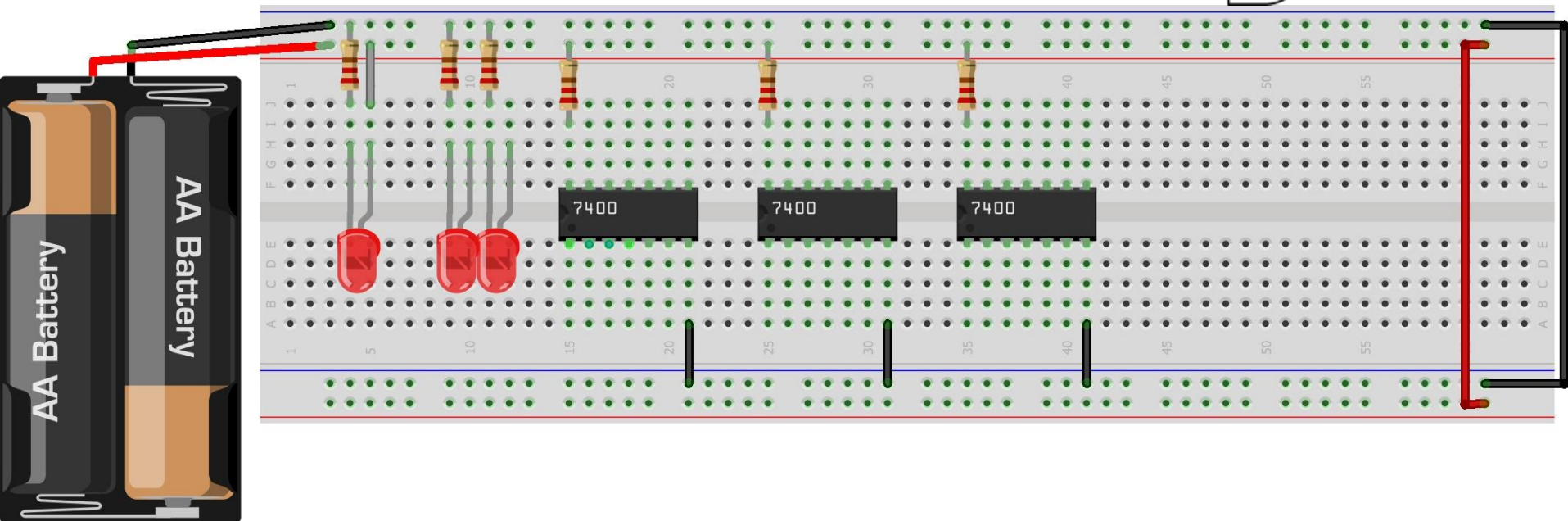 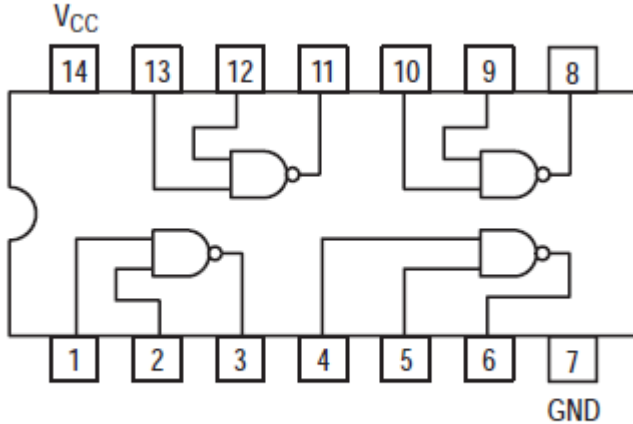

Build the Full Adder!

 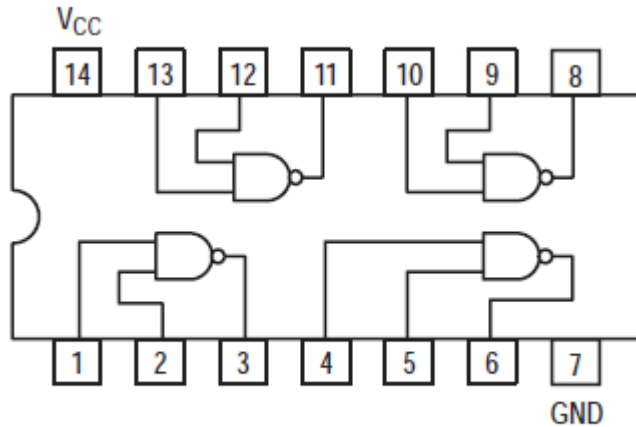

Now what?

<http://hackaday.com>

<http://sparkfun.com>

<http://adafruit.com>

<http://arduino.cc>

<http://fubarlabs.org>